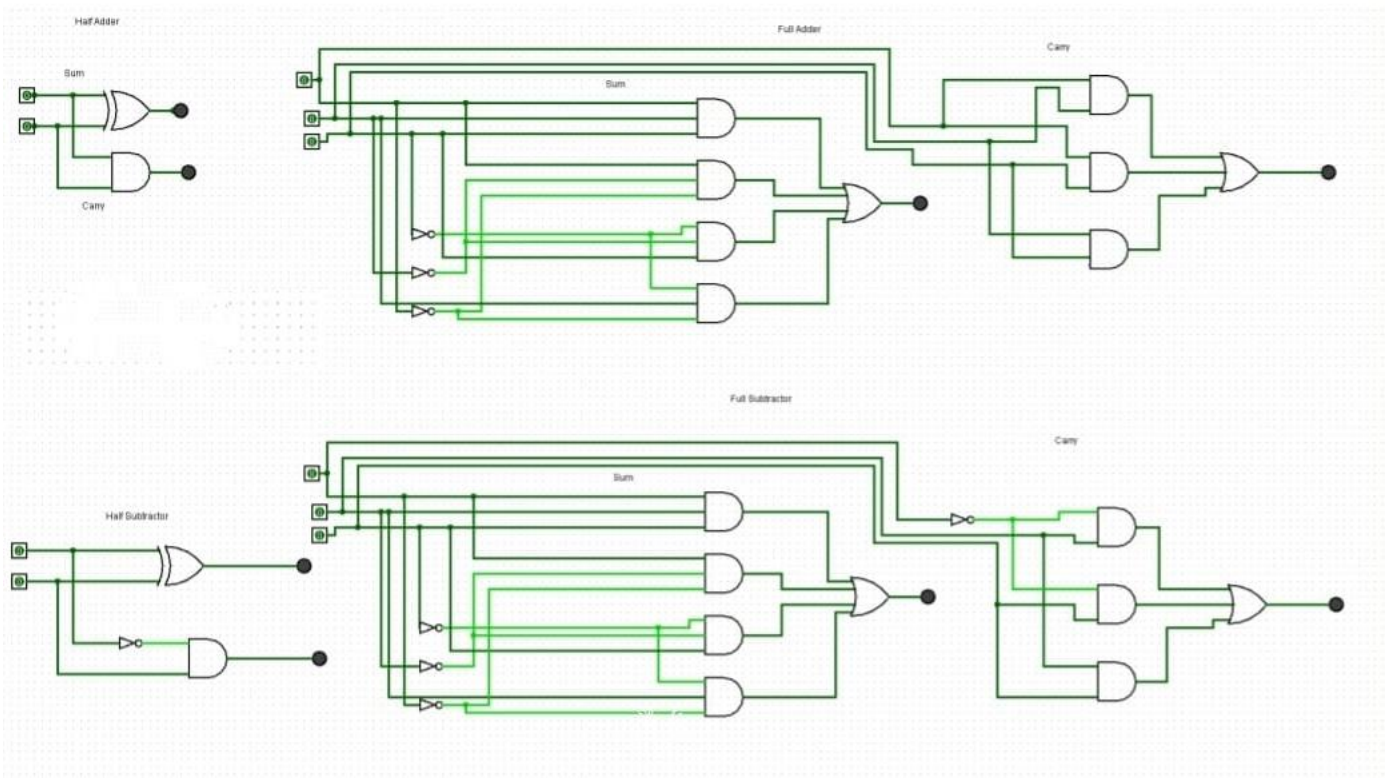


MPL ASSIGNMENT NO. 2

ADDER AND SUBTRACTOR(HALF AND FULL)



Atharva Yadav S23-127